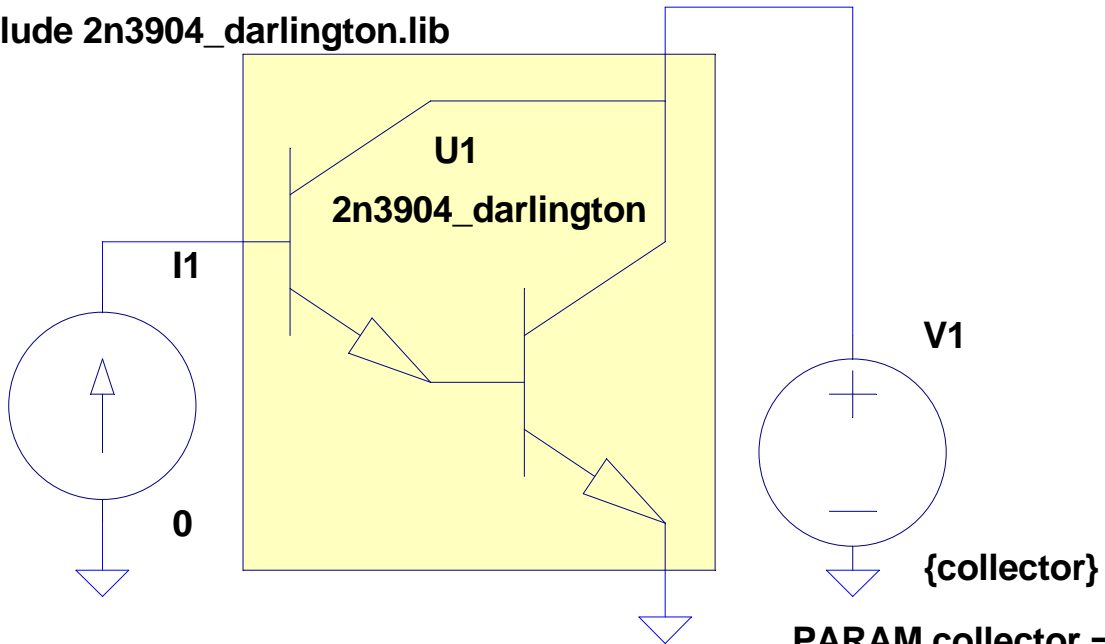


**TRANSCEIVER CW F8EOZ - DARLINGTON NPN 2N3904 CURVE - V 13/11/2012 09:45**

**Transfer characteristic curve: Collector current vs Base current**

**$I_c = f(I_b) \mid V_{ce} = \text{constant slope} = \beta$**

**.include 2n3904\_darlington.lib**



**.dc I1 0 50n 0.0001n  
.options plotwinsize=0**

**.PARAM collector = 10.708426**